ALL PROGRAMMABLE





Digital Design Tutorial

Xilinx University Program




Digital Clock

- > 实验介绍
- > 演示

实验介绍

数字钟是一个以秒为单位的计时器,可以在数码管上显示"秒"和"分"。通过将FPGA时钟分频,得到1秒为周期的时钟信号作为脉冲激励。同时使用计数电路74LS90和与门电路74LS08搭建模60计数器。并将最终的时间通过数码管模块显示在板卡的数码管上。

SN74LS90

 


Input				Output			
R0_1	R0_2	R9_1	R9_2	qa	qb	qc	qd
Н	Н	L	X	L	L	L	L
Н	Н	X	L	L	L	L	L
X	X	Н	Н	Н	L	L	Н
X	L	X	L	Count			
L	X	L	X				
L	L	X	X				
X	X	L	L				

H=High-Level L=Low-Level X=Don't Care


SN74LS08

Input		Output		
a1	b1	y1		
L	X	L		
X	L	L		
Н	Н	Н		

H=High-Level L=Low-Level X=Don't Care

 

模60计数器

 

Vivado Flow Overview

- > Step 1: Create New Project
- > Step 2: Add Source Files and IP
- > Step 3: Generate Bitstream
- > Step 4: Download Bitstream and Verify Functionality

Step 1: Create New Project

- Specify Project Name
- Specify Project Type
- > Import/Create Source files
- > Specify Device to be used

Step 2: Add Source Files and IP

- > Create Block Design
- ➤ Open IP Catalog
- **▶** Add IP Repository
- > Add IP to the project
- > Create HDL wrapper

Step 3: Generate Bitstream

- > Add Pin Constraints
- > Generate Bitstream
- **▶** Check your Timing in Design Runs Window

Step 4: Download Bitstream and Verify Functionality

- ➤ Make sure your board is connected to your PC
- > Turn on your FPGA board
- ➤ Open Hardware Manager
- > Program Device
- > Verify Functionality on Hardware

总结

- ➤ 创建Block Design
- ➤ 在Block Design内添加IP
- ▶ 74LS90和74LS08

